Waveforms in CCM

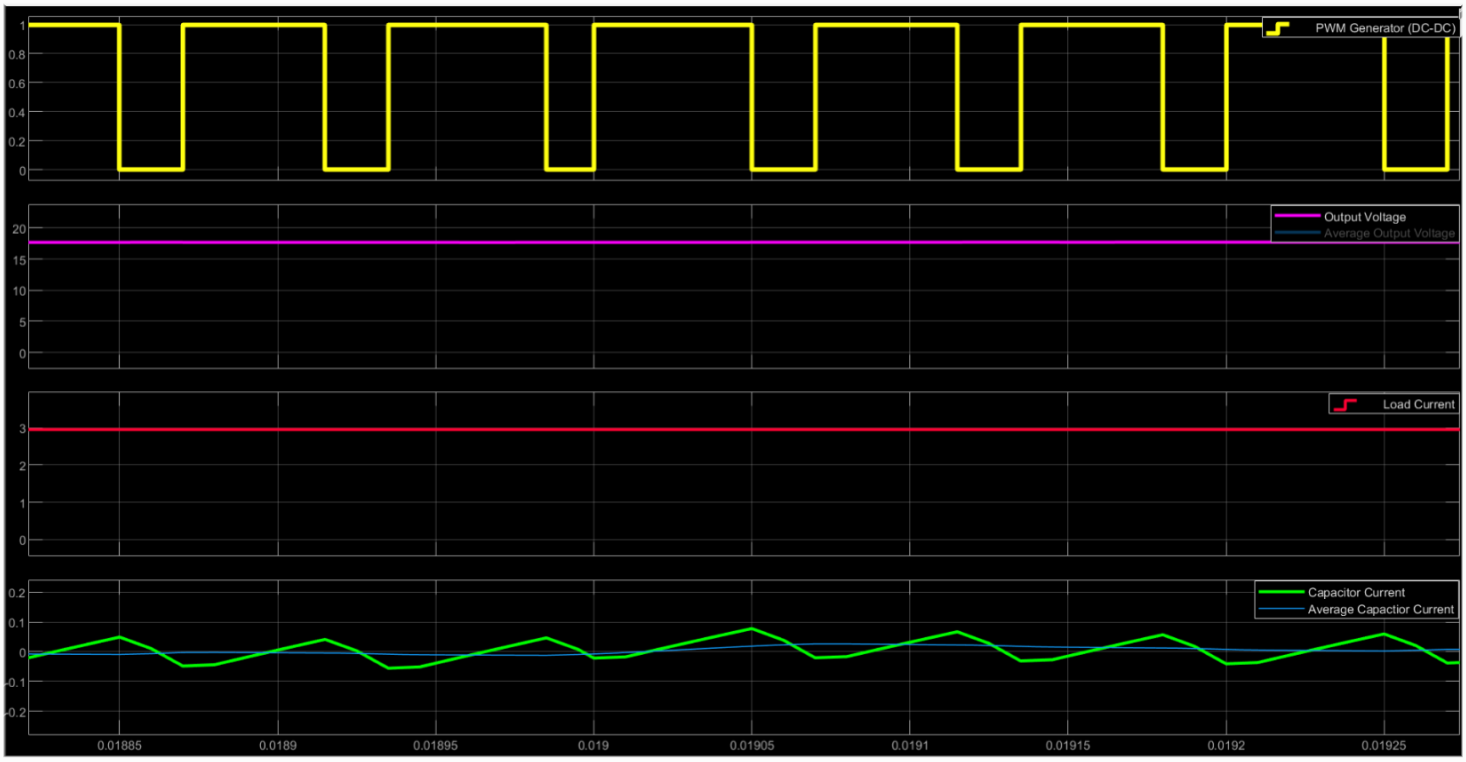

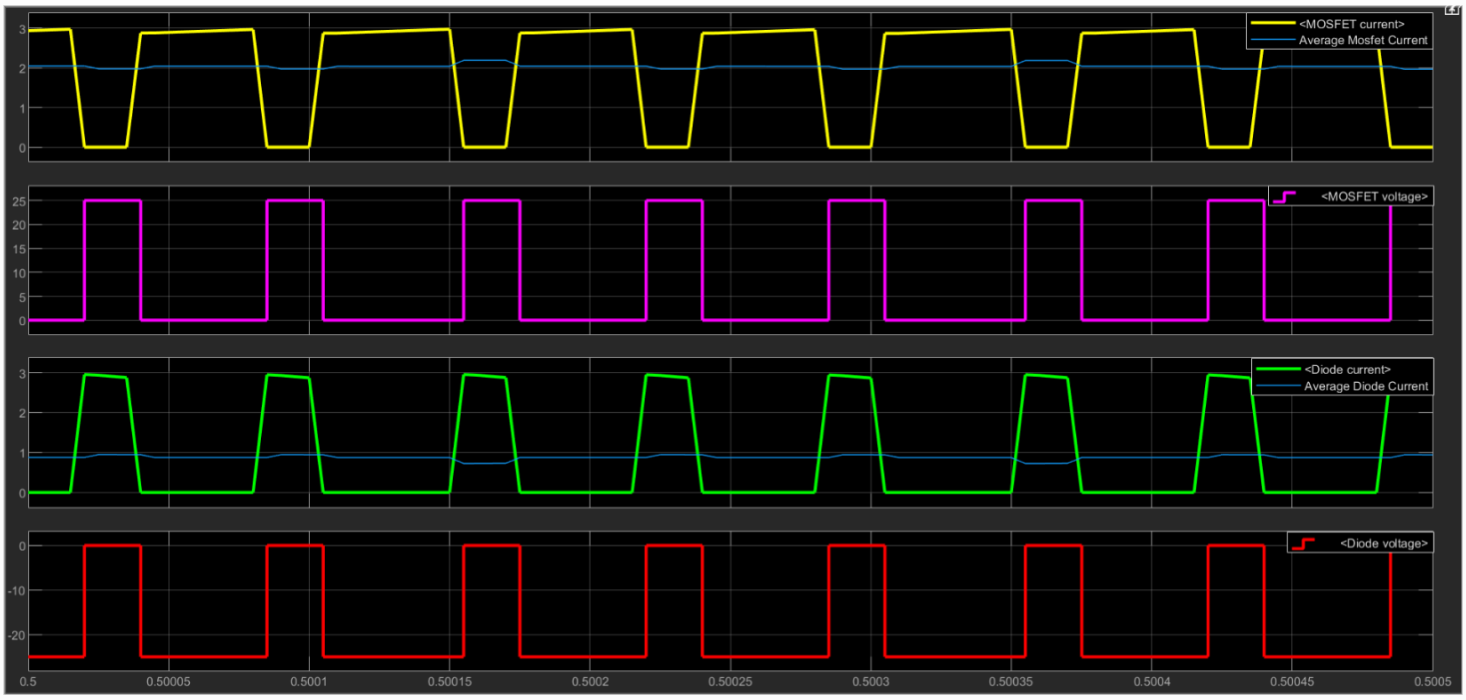

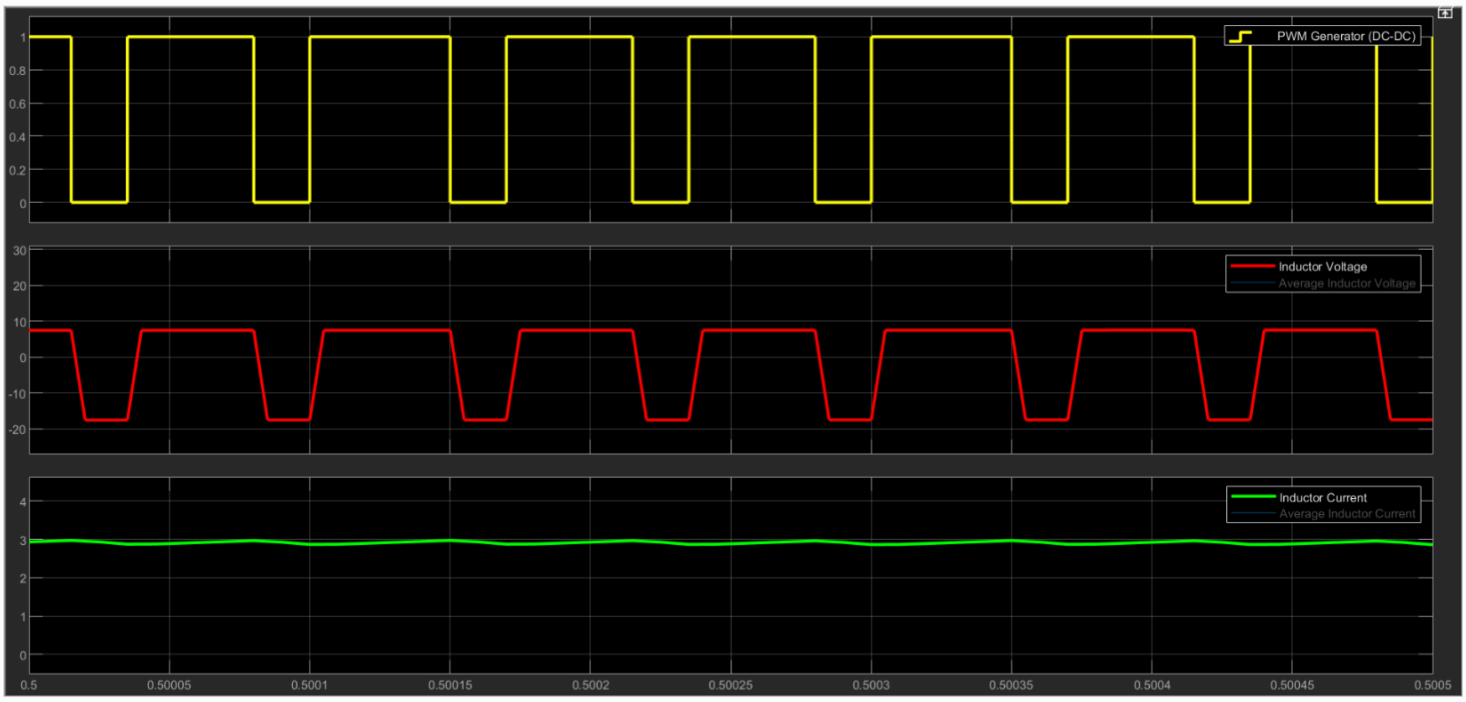

Waveform in BCM (boundary conduction mode)

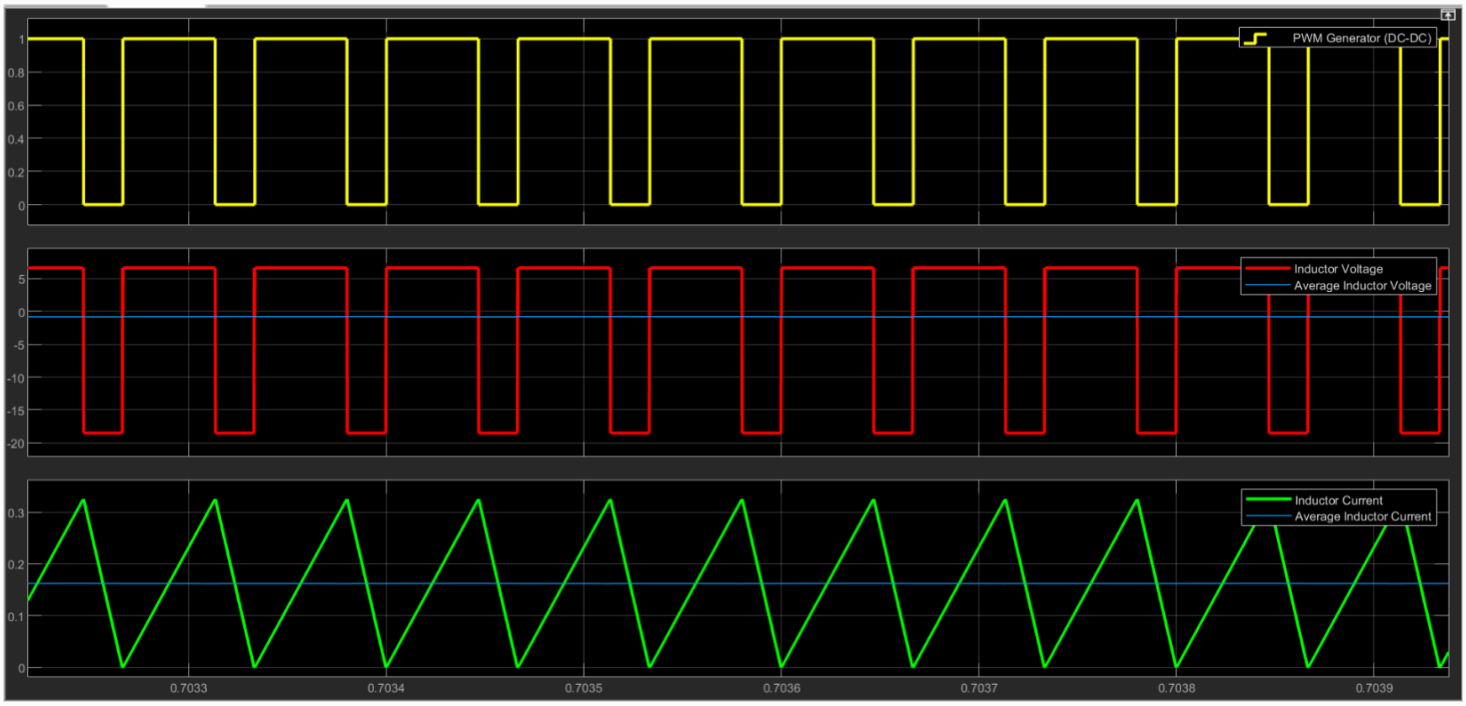

Waveform in DCM (discontinous conduction mode)

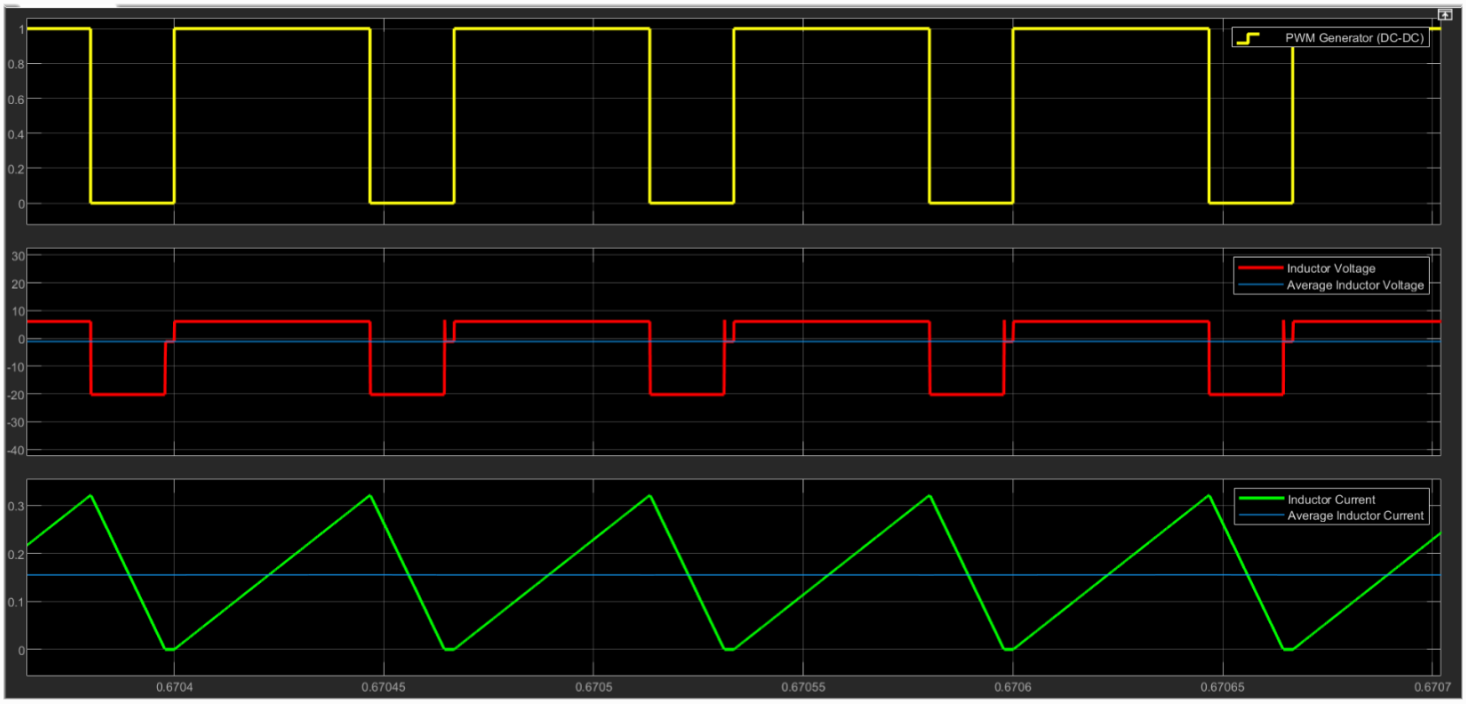
PWM Generator (DC-DC)
1
0.8
0.6
0.4
0.2
0
Inductor Voltage
Average Inductor Voltage
30
20
10
0
-10
-20
-30
-40
Inductor Current
Average Inductor Current
0.3
0.2
0.1
0
0.6704
0.67045
0.6705
0.67055
0.6706
0.67065
0.6707